Coding group #	21
Student 1	
NAME	Theodore Janson
ID	260868223
Student 2	
NAME	Edin Huskic
ID	260795559
Student 3 (if applicable)	
NAME	
ID	

Question 1 (2 marks)

Give the VHDL code that you wrote for the clock divider.

What is the value of \$T\$ that you used? T= 50000000

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity g21_clock_divider is
Port (
enable : in std logic;
reset : in std_logic;
clk : in std_logic;
en out : out std logic
);
 end g21_clock_divider;
architecture behavioral of g21 clock divider is
signal T : integer := 50000000;
signal count: integer:= T-1;
process(clk, enable, reset)
BEGIN
if reset = '0' then
    en out <= '0';
elsif enable = '1' then
    if rising_edge(clk) then
        if count = 0 then
           en out <= '1';
            count <= 50000000-1;
    else
        en_out <= '0';
        count <= (count - 1);
    end if;
end if;
end if;
end process;
end behavioral;
```

McGill University Page 1 of 3

Question 2 (2 marks)


Give the VHDL code that you wrote for the 3-bit counter..

```
library IEEE;
 use IEEE.STD LOGIC 1164.ALL;
 use IEEE.NUMERIC STD.ALL;
 use IEEE.STD LOGIC UNSIGNED.ALL;
mentity g21 counter is
Port ( enable : in std logic;
 reset : in std logic;
 clk : in std logic;
 count : out std logic vector (2 downto 0)
end g21 counter;
parchitecture behavioral of g21_counter is
 signal temp : std logic vector(2 downto 0) := "000";
□BEGIN
process(clk, enable, reset)
 BEGIN
if reset = '0' then
     count <= "000";
     temp <= "000";
⊨elsif enable = '1' then
     if rising edge(clk) then
         if temp = "111" then
         temp <= "000";
         count <= temp;</pre>
else
         temp <= temp + "1";
         count <= temp;</pre>
         end if;
     end if;
 end if;
 end process;
 end behavioral;
```

Question 3 (2 marks)

Show a representative simulation plot of your $gNN_counter$ circuit. You can simply include a snapshot from the waveform that you obtained from ModelSim. In order to fully capture all the signals from the waveform, you can adjust the display range using the magnifier icons.

McGill University Page 2 of 3

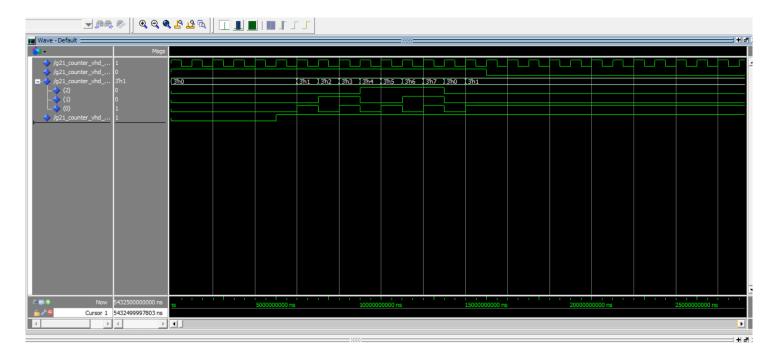

McGill University Page 3 of 3